

Sirindhorn International Institute of Technology

Thammasat University at Rangsit

School of Information, Computer and Communication Technology

ECS 371: Solution for Problem Set 2

Semester/Year: 1/2009

Course Title: Digital Circuits

Instructor: Dr. Prapun Suksompong (prapun@siit.tu.ac.th)

Course Web Site: <http://www.siit.tu.ac.th/prapun/ecs371/>

Due date: July 2, 2009 (Thursday)

Please submit your homework to the instructor 3 minutes BEFORE your class starts.

Instructions

- The questions are assigned from the following textbook:
Thomas L. Floyd, [*Digital Fundamentals*](#), 10th Edition, Pearson Education International (2009).
- Only TWO of the problems will be graded. Of course, you do not know which problems will be selected; so you should work on all of them.
- Late submission will not be accepted.
- Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

Chapter 4

6. Find the value of X for all possible values of the variables.

(a) $X = (A + B)C + B$

(b) $X = (\overline{A + B})C$

(c) $X = A\overline{B}C + AB$

(d) $X = (A + B)(\overline{A} + B)$

(e) $X = (A + BC)(\overline{B} + \overline{C})$

6. (a) $X = (A + B)C + B$

A	B	C	$A + B$	$(A + B)C$	X
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	1	1	1
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	1	1

(b) $X = \overline{(A+B)}C$

A	B	C	$\overline{A+B}$	X
0	0	0	1	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

(c) $X = \overline{A}BC + AB$

A	B	C	$\overline{A}BC$	AB	X
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	1	1
1	1	1	0	1	1


(d) $X = (A+B)(\overline{A}+B)$

A	B	A+B	$\overline{A}+B$	X
0	0	0	1	0
0	1	1	1	1
1	0	1	0	0
1	1	1	1	1

(e) $X = (A+BC)(\overline{B}+\overline{C})$

A	B	C	A+BC	$\overline{B}+\overline{C}$	X
0	0	0	0	1	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	1	1
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	0	0

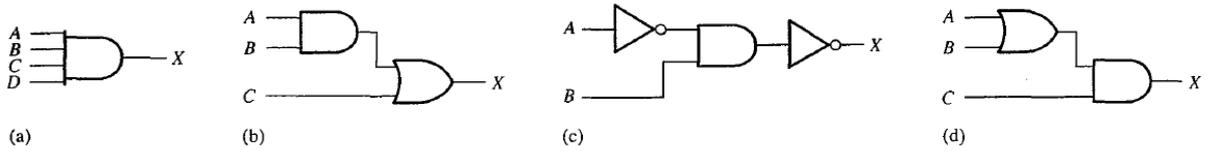13. Write the Boolean expression for each of the logic circuits in Figure 4-54.



13. See Figure 4-1.

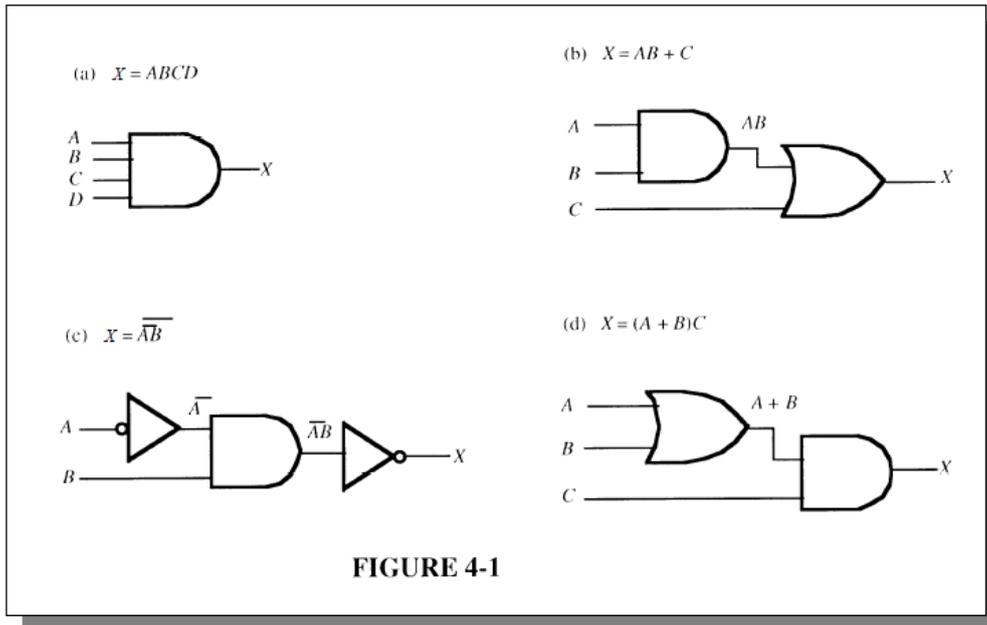


FIGURE 4-1

15. Draw the logic circuit represented by each expression:

- (a) $\overline{AB} + \overline{AB}$ (b) $AB + \overline{A}\overline{B} + \overline{A}BC$
 (c) $\overline{A}B(C + \overline{D})$ (d) $A + B[C + D(B + \overline{C})]$

15. See Figure 4-3.

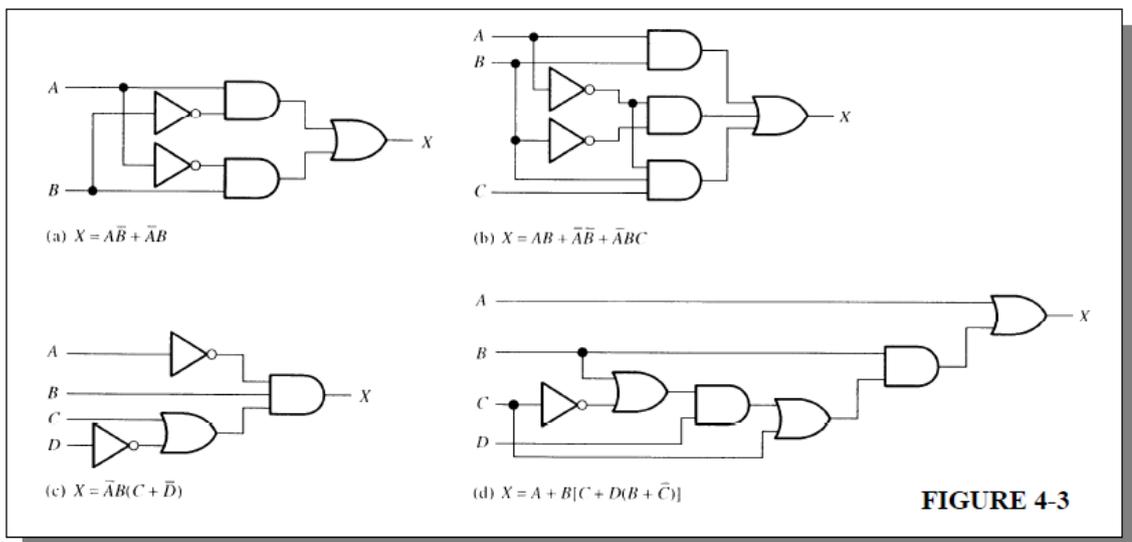


FIGURE 4-3


20. Using Boolean algebra, simplify the following expressions:

- (a) $(A + \bar{B})(A + C)$ (b) $\bar{A}B + \bar{A}B\bar{C} + \bar{A}BCD + \bar{A}B\bar{C}\bar{D}E$
 (c) $AB + \bar{A}BC + A$ (d) $(A + \bar{A})(AB + ABC)$
 (e) $AB + (\bar{A} + \bar{B})C + AB$


20. (a) $(A + \bar{B})(A + C) = AA + AC + \bar{A}B + \bar{B}C = A + AC + \bar{A}B + \bar{B}C$
 $= A(1 + C + \bar{B}) + \bar{B}C = A(1) + \bar{B}C = A + \bar{B}C$
 (b) $\bar{A}B + \bar{A}B\bar{C} + \bar{A}BCD + \bar{A}B\bar{C}\bar{D}E = \bar{A}B(1 + \bar{C} + CD + \bar{C}\bar{D}E) = \bar{A}B(1)$
 $= \bar{A}B$
 (c) $AB + \bar{A}BC + A = AB + (\bar{A} + \bar{B})C + A = AB + \bar{A}C + \bar{B}C + A$
 $A(B + 1) + \bar{A}C + \bar{B}C = A + \bar{A}C + \bar{B}C = A + C + \bar{B}C = A + C(1 + \bar{B})$
 $= A + C$
 (d) $(A + \bar{A})(AB + ABC) = AAB + AABC + \bar{A}AB + \bar{A}ABC$
 $= AB + ABC + 0 + 0 = AB(1 + C) = AB$
 (e) $AB + (\bar{A} + \bar{B})C + AB = AB + \bar{A}C + \bar{B}C + AB = AB + (\bar{A} + \bar{B})C$
 $= AB + \bar{A}BC = AB + C$

22. Determine which of the logic circuits in Figure 4-56 are equivalent.


FIGURE 4-56

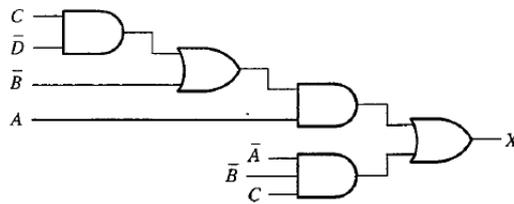


(a)

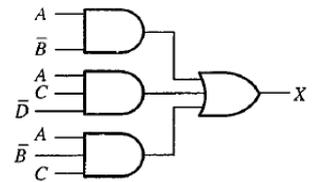

(b)

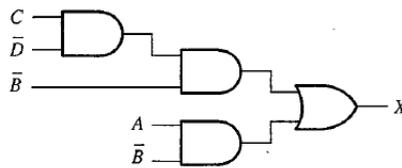


(c)

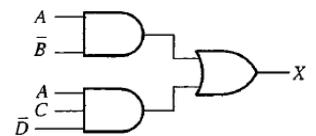

(d)


22. First develop the Boolean expression for the output of each gate network and simplify.

(a) See Figure 4-5.

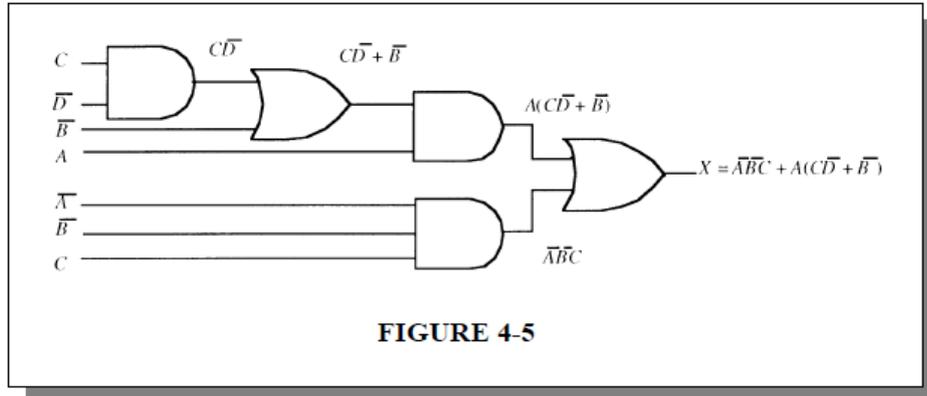


$$\begin{aligned} X &= \overline{A}B\overline{C} + A(C\overline{D} + \overline{B}) = \overline{A}B\overline{C} + AC\overline{D} + A\overline{B} = \overline{B}(A + \overline{A}C) + AC\overline{D} \\ &= \overline{B}(A + C) + AC\overline{D} = \overline{A}B + \overline{B}C + AC\overline{D} \end{aligned}$$

(b) See Figure 4-6.

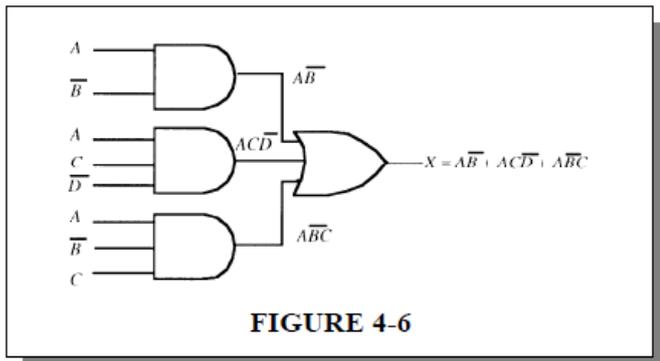


$$X = A\overline{B} + AC\overline{D} + A\overline{B}C = A\overline{B}(1 + C) + AC\overline{D} = A\overline{B} + AC\overline{D}$$

(c) See Figure 4-7.

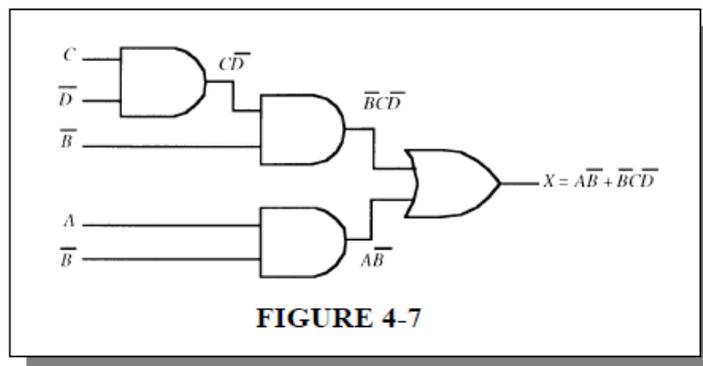

$$X = A\overline{B} + \overline{B}C\overline{D} \text{ No further simplification is possible.}$$

(d) See Figure 4-8.

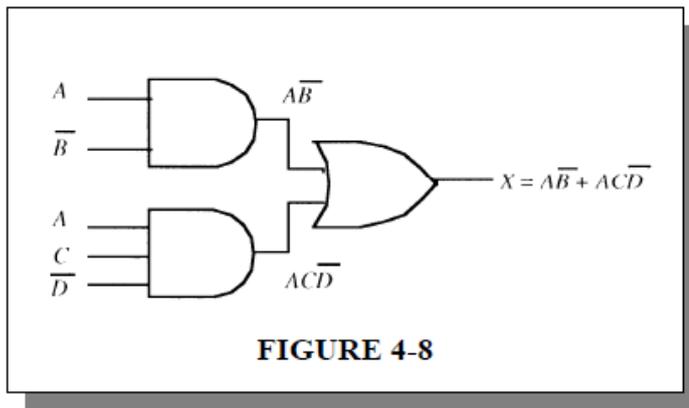

$X = A\overline{B} + AC\overline{D}$ No further simplification is possible.

Therefore, (b) and (d) are equivalent.