

Sirindhorn International Institute of Technology

Thammasat University at Rangsit

School of Information, Computer and Communication Technology

ECS 371: Problem Set 2

Semester/Year: 1/2009

Course Title: Digital Circuits

Instructor: Dr. Prapun Suksumpong (prapun@siit.tu.ac.th)

Course Web Site: <http://www.siit.tu.ac.th/prapun/ecs371/>

Due date: July 2, 2009 (Thursday)

Please submit your homework to the instructor 3 minutes BEFORE your class starts.

Instructions

1. The questions are assigned from the following textbook:

Thomas L. Floyd, [*Digital Fundamentals*](#), 10th Edition, Pearson Education International (2009).

2. Only ONE of the problems will be graded. Of course, you do not know which problems will be selected; so you should work on all of them.
3. Late submission will not be accepted.
4. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

Chapter 4

- 6(b,c,d,e), 13, 15, 20, 22

6. Find the value of X for all possible values of the variables.

(a) $X = (A + B)C + B$


(b) $X = (\overline{A + B})C$

(c) $X = A\overline{B}C + AB$


(d) $X = (A + B)(\overline{A} + B)$

(e) $X = (A + BC)(\overline{B} + \overline{C})$

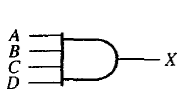
13. Write the Boolean expression for each of the logic circuits in Figure 4–54.




(a)

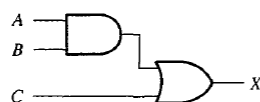

(b)

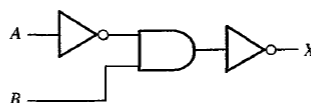

(c)

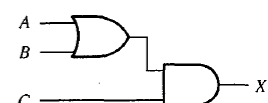

(d)

15. Draw the logic circuit represented by each expression:


- (a) $A\bar{B} + \bar{A}B$ (b) $AB + \bar{A}\bar{B} + \bar{A}BC$
 (c) $\bar{A}B(C + \bar{D})$ (d) $A + B[C + D(B + \bar{C})]$

20. Using Boolean algebra, simplify the following expressions:


- (a) $(A + \bar{B})(A + C)$ (b) $\bar{A}B + \bar{A}B\bar{C} + \bar{A}BCD + \bar{A}B\bar{C}\bar{D}E$
 (c) $AB + \bar{A}BC + A$ (d) $(A + \bar{A})(AB + ABC)$
 (e) $AB + (\bar{A} + \bar{B})C + AB$

22. Determine which of the logic circuits in Figure 4-56 are equivalent.


FIGURE 4-56

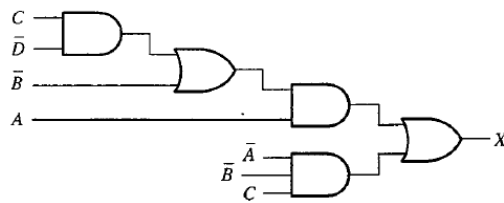


(a)

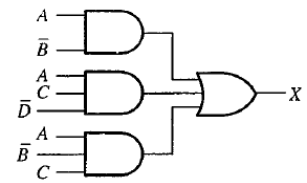

(b)

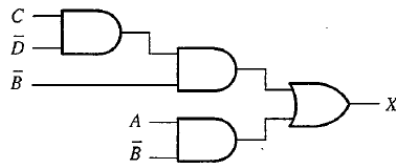

(c)

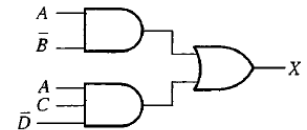

(d)