

Sirindhorn International Institute of Technology  
Thammasat University at Rangsit  
School of Information, Computer and Communication Technology

## ECS 371: Solution for Problem Set 4

**Semester/Year:** 1/2009

**Course Title:** Digital Circuits

**Instructor:** Dr. Prapun Suksompong ([prapun@siit.tu.ac.th](mailto:prapun@siit.tu.ac.th))

**Course Web Site:** <http://www.siiit.tu.ac.th/prapun/ecs371/>

### **Due date: July 16, 2009 (Thursday)**


Please submit your homework to the instructor 3 minutes BEFORE your class starts.

### **Instructions**

1. The questions are assigned from the following textbook:  
  
Thomas L. Floyd, [\*Digital Fundamentals\*](#), 10<sup>th</sup> Edition, Pearson Education International (2009).
2. Only ONE of the problems will be graded. Of course, you do not know which problems will be selected; so you should work on all of them.
3. Late submission will not be accepted.
4. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

### **Chapter 5**

- 4(b,c,e), 20a, 22a, 56
4. Write the output expression for each circuit as it appears in Figure 5–56 and then change each circuit to an equivalent AND-OR configuration.

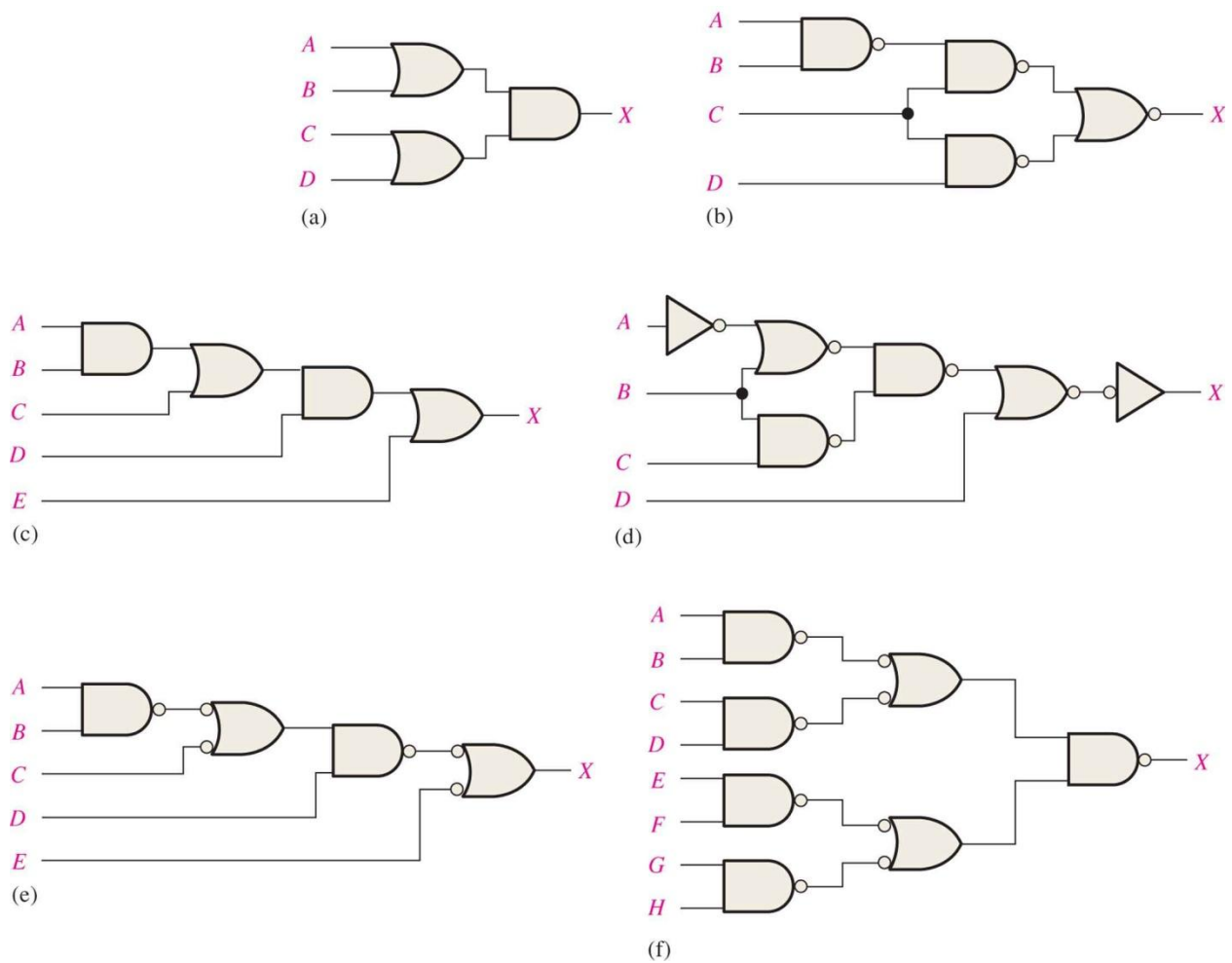

**FIGURE 5-56**

4. See Figure 5-2 for the circuit corresponding to each expression.

(a)  $X = (A + B)(C + D) = AC + AD + BC + BD$







(b)  $X = \overline{\overline{ABC} + \overline{CD}} = \overline{\overline{ABC}}(\overline{CD}) = (\overline{A} + \overline{B})\overline{CD} = \overline{A}CD + \overline{B}CD$

(c)  $X = (AB + C)D + E = ABD + CD + E$

(d)  $X = \overline{\overline{(A+B)(BC)} + D} = \overline{\overline{(A+B)(BC)}} + D = \overline{\overline{A} + \overline{B} + \overline{BC}} + D = \overline{\overline{A} + \overline{B}} + D = \overline{\overline{A} + \overline{B}} + D$

(e)  $X = \overline{\overline{(AB+C)D} + \overline{E}} = \overline{\overline{(AB+C)D}} + \overline{\overline{E}} = ABD + \overline{CD} + \overline{E}$

(f)  $X = \overline{\overline{(AB+CD)(EF+GH)}} = \overline{\overline{(AB+CD)}(\overline{EF+GH})} = \overline{\overline{(AB+CD)} + \overline{(EF+GH)}}$   
 $= \overline{\overline{(AB)}(\overline{CD})} + \overline{\overline{(EF)}(\overline{GH})}$   
 $= (\overline{A} + \overline{B})(\overline{C} + \overline{D}) + (\overline{E} + \overline{F})(\overline{G} + \overline{H}) = \overline{A}\overline{C} + \overline{B}\overline{C} + \overline{A}\overline{D} + \overline{B}\overline{D} + \overline{E}\overline{G} + \overline{F}\overline{G} + \overline{E}\overline{H} + \overline{F}\overline{H}$

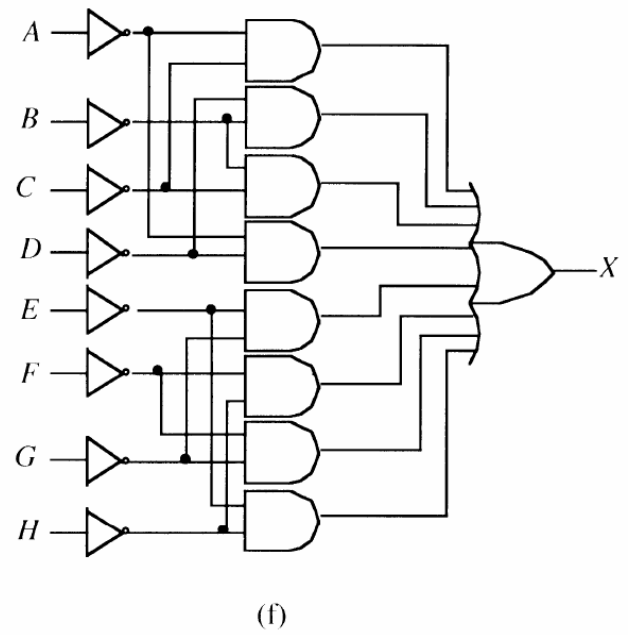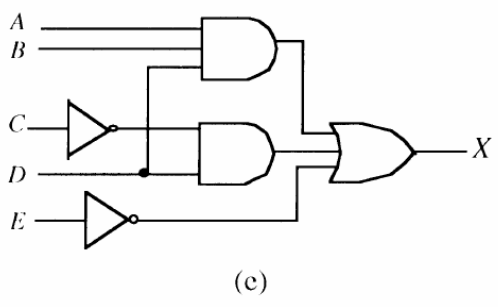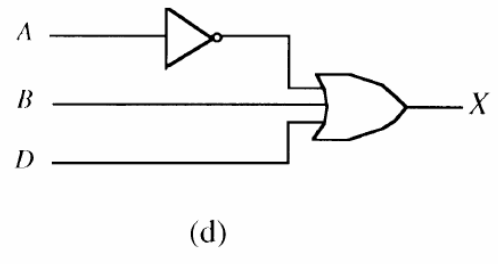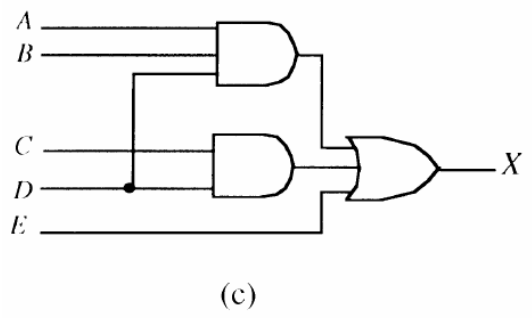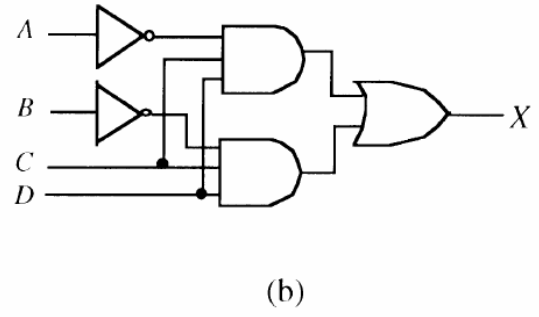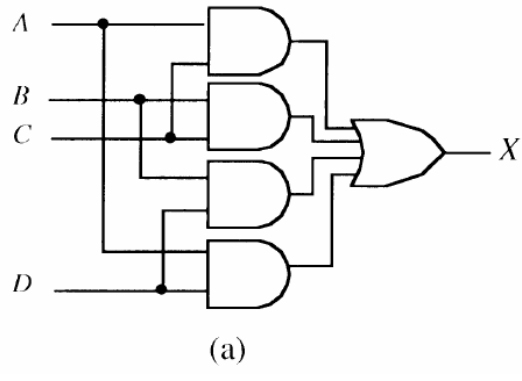

**FIGURE 5-2**

**20.** Implement the logic circuits in Figure 5-54 using only NAND gates.

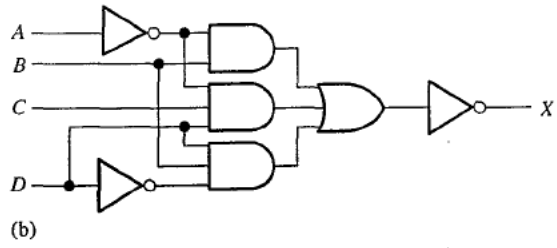
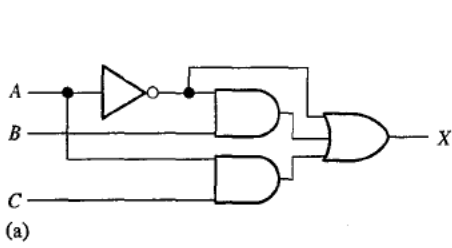


FIGURE 5-54

20. See Figure 5-20.

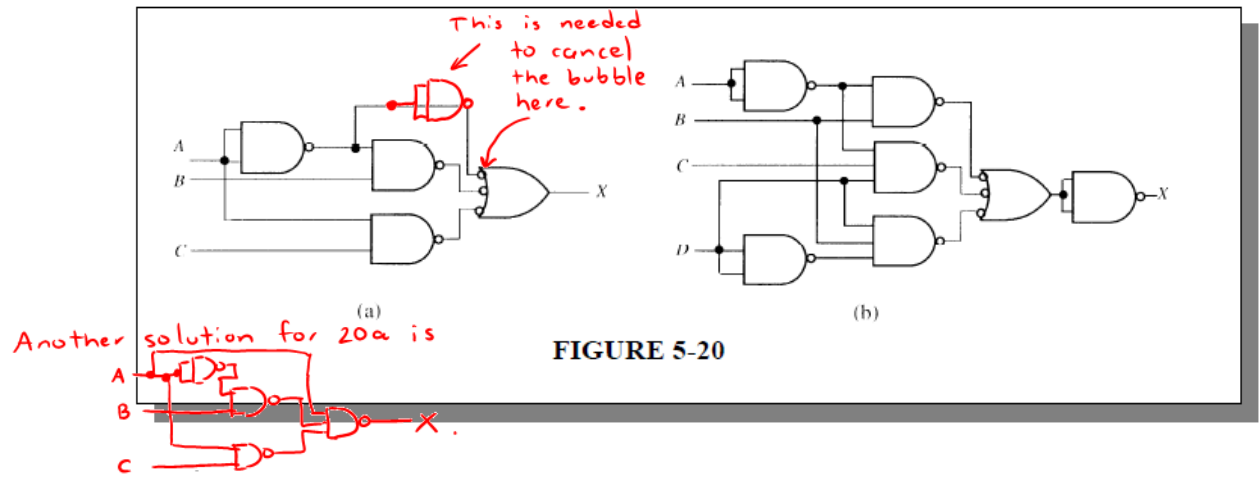


FIGURE 5-20

22. Repeat Problem 20 using only NOR gates.

22. See Figure 5-22.

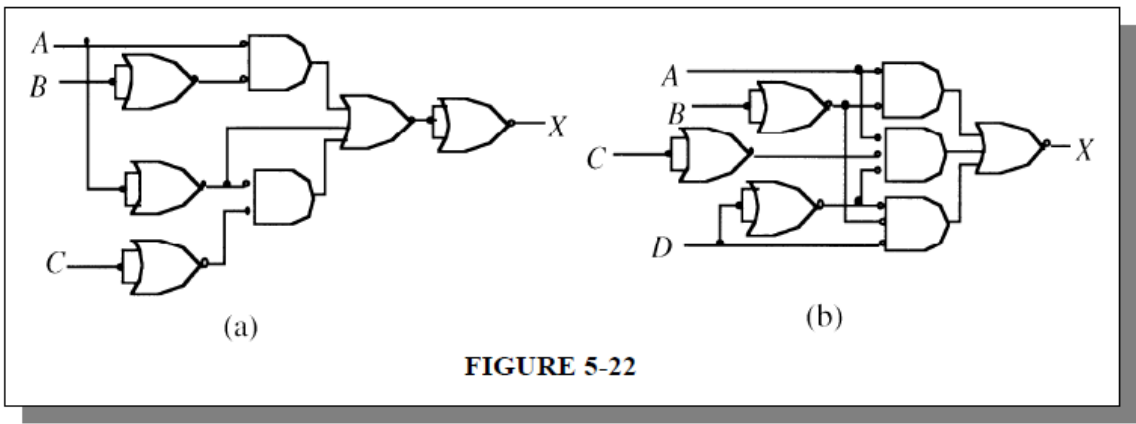


FIGURE 5-22

56. Design a logic circuit to produce a HIGH output only if the input, represented by a 4-bit binary number, is greater than twelve or less than three. First develop the truth table and then draw the logic diagram.

56.

$A_3$	$A_2$	$A_1$	$A_0$	$X$
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

See Figure 5-68.

