

Sirindhorn International Institute of Technology
Thammasat University at Rangsit
School of Information, Computer and Communication Technology

ECS 371: Problem Set 4

Semester/Year: 1/2009

Course Title: Digital Circuits

Instructor: Dr. Prapun Suksompong (prapun@siit.tu.ac.th)

Course Web Site: <http://www.siiit.tu.ac.th/prapun/ecs371/>

Due date: July 16, 2009 (Thursday)

Please submit your homework to the instructor 3 minutes BEFORE your class starts.

Instructions

1. The questions are assigned from the following textbook:

Thomas L. Floyd, [*Digital Fundamentals*](#), 10th Edition, Pearson Education International (2009).
2. Only ONE of the problems will be graded. Of course, you do not know which problems will be selected; so you should work on all of them.
3. Late submission will not be accepted.
4. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

Chapter 5

- Please submit your solutions for the following questions: 4(b,c,e), 20a, 22a, 56
4. Write the output expression for each circuit as it appears in Figure 5–56 and then change each circuit to an equivalent AND-OR configuration.

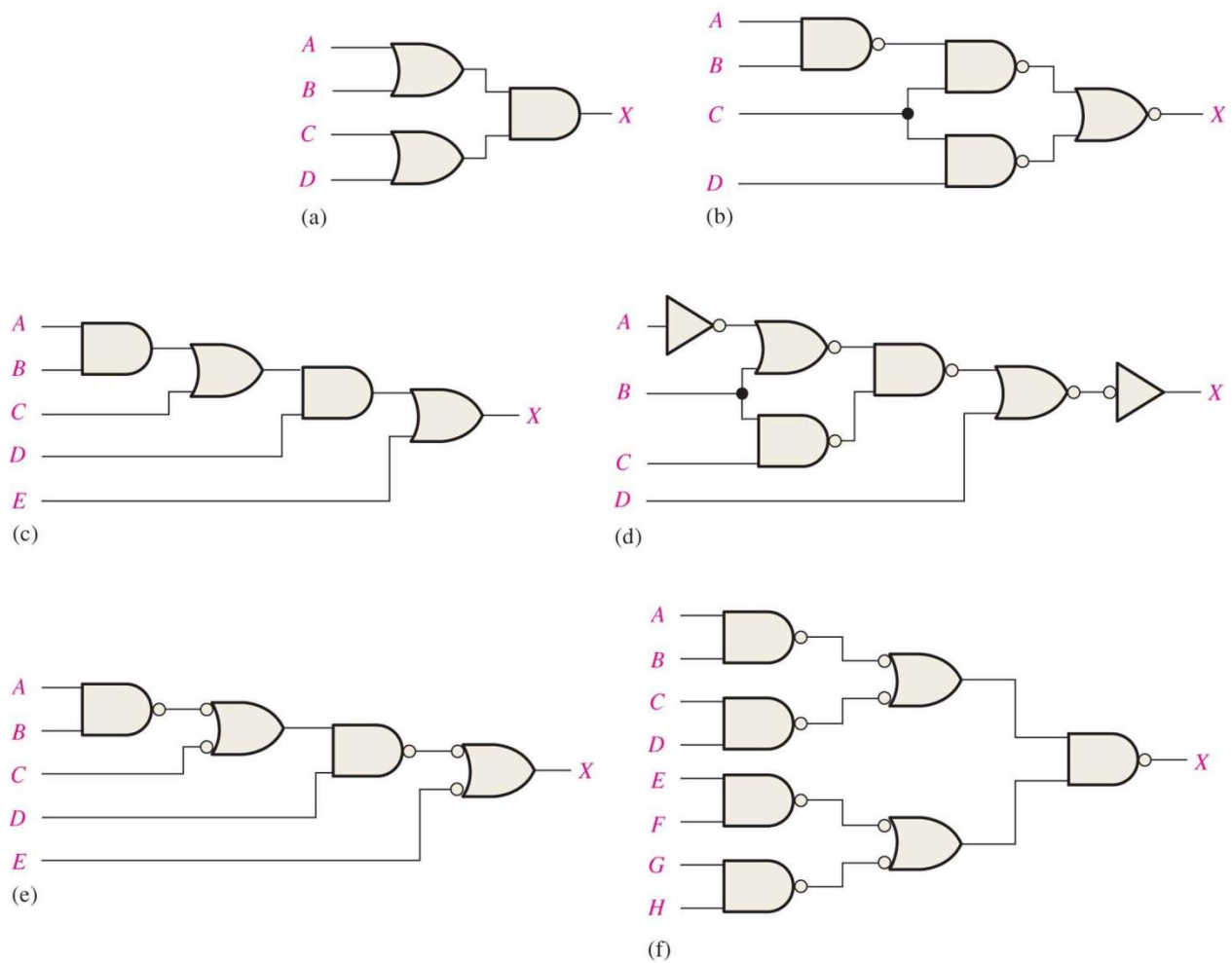


FIGURE 5-56

20. Implement the logic circuits in Figure 5-54 using only NAND gates.


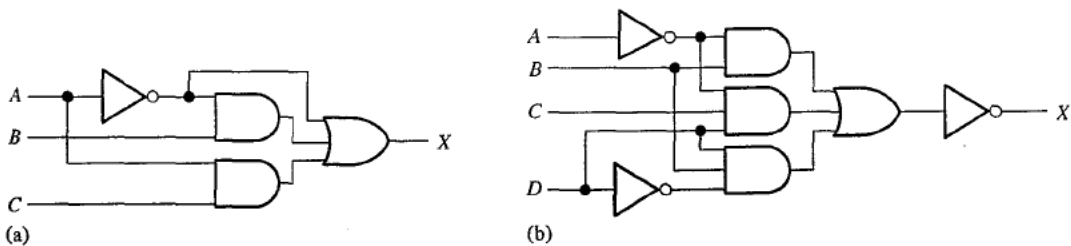


FIGURE 5-54

22. Repeat Problem 20 using only NOR gates.

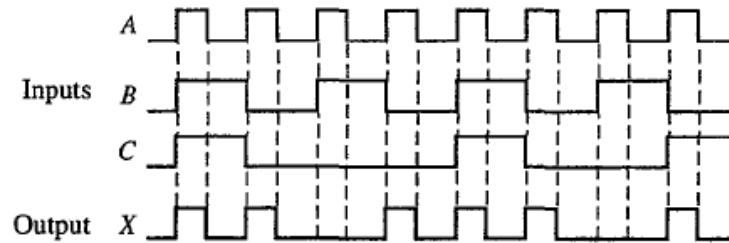30. For the input waveforms in Figure 5-61, what logic circuit will generate the output waveform shown?



▲ FIGURE 5-61

56. Design a logic circuit to produce a HIGH output only if the input, represented by a 4-bit binary number, is greater than twelve or less than three. First develop the truth table and then draw the logic diagram.