

Sirindhorn International Institute of Technology
Thammasat University at Rangsit
School of Information, Computer and Communication Technology

ECS 371: Problem Set 6

Semester/Year: 1/2009

Course Title: Digital Circuits

Instructor: Dr. Prapun Suksompong (prapun@siit.tu.ac.th)

Course Web Site: <http://www.siit.tu.ac.th/prapun/ecs371/>

Due date: August 19, 2009 (Wednesday)

Instructions

1. The questions are assigned from the following textbook:

Thomas L. Floyd, [*Digital Fundamentals*](#), 10th Edition, Pearson Education International (2009).



2. Only ONE of the problems will be graded. Of course, you do not know which problems will be selected; so you should work on all of them.
3. Late submission will not be accepted.
4. **Write down all the steps** that you have done to obtain your answers. You may not get full credit even when your answer is correct without showing how you get your answer.

Chapter 7

- Please submit your solutions for the following questions: 2, 4, 8, 10, 12, 14, 18

1. If the waveforms in Figure 7-72 are applied to an active-LOW input S-R latch, draw the resulting Q output waveform in relation to the inputs. Assume that Q starts LOW.


► FIGURE 7-72

  


2. Solve Problem 1 for the input waveforms in Figure 7-73 applied to an active-HIGH S-R latch.



 4. For a gated S-R latch, determine the Q and \bar{Q} outputs for the inputs in Figure 7-75. Show them in proper relation to the enable input. Assume that Q starts LOW.




 8. Two edge-triggered S-R flip-flops are shown in Figure 7-79. If the inputs are as shown, draw the Q output of each flip-flop relative to the clock, and explain the difference between the two. The flip-flops are initially RESET.



▷ **FIGURE 7-79**

 10. Draw the Q output relative to the clock for a D flip-flop with the inputs as shown in Figure 7-81. Assume positive edge-triggering and Q initially LOW.



18. Solve Problem 17 with the same J and K inputs but with the \overline{PRE} and \overline{CLR} inputs as shown in Figure 7-89 in relation to the clock.

FIGURE 7-89

