

Announcement

HW 1 : Due on Thursday.
before class


Lecture Notes from last time are
already on class website.


Scanned version is posted.


Review


* Logic Circuit \leftrightarrow Boolean
Expression


Ex.  $A \cdot B$

 $A + B$

 $\bar{A} \cdot \bar{B}$ (Negative-AND)

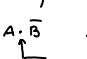 $A \cdot \bar{B}$

 is not a gate

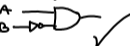

$A \cdot (\bar{B})$ is not the same as $\overline{(A \cdot B)}$

↑ Do the B complement first and then AND with the A

↑ Do the AND first and then complement the rest.

Ex. Find the value of X
for all possible values
of the variables when

$$X = (A+B) \cdot C + B$$

A	B	C	(A+B) · C	+ B
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	0
1	1	1	1	1

Ex Draw the logic circuit
represented by

$$X = (A+B) \cdot C + B$$



Ex. Simplify

$$\begin{aligned} (A+B) \cdot C + B &= AC + BC + B \\ &= AC + BC + B \cdot 1 \\ &= AC + B(C+1) \end{aligned}$$

$$= AC + B \cdot 1$$

$$= AC + B$$

Ex. $A \cdot B + A(B+C) = A \cdot B + AB + AC$

(A.M.)

$$= \overbrace{AB}^{AB} + AC$$

$$= A(B+C)$$

Ex. Check

$AB +$

by tru

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1



Advantage :




Disadvantage :

that
 $A(B+C) = A(B+C)$
 in table.
 $A(B+C) = A(B+C)$
 0 0 0 0
 0 0 0 1
 0 0 0 1
 0 0 0 1
 0 0 0 0
 0 1 1 1
 1 1 1 1
 1 1 1 1
 same!
 A.M. quick (usually)
 simple
 Need to know laws/
 rules.

② Truth table
 Advantage: straight-forward
 Disadvantage: Tedious
 ③ K-map ← Alternative way to write a truth table.
 Back to "new material"
 Ex. $X \text{ NAND } 1 = \bar{X}$
 $\bar{X \cdot 1} = \bar{X}$
 Ex. $X \text{ NOR } 0 = \bar{X}$
 $\overline{X + 0} = \bar{X}$

Ex. $X \text{ NAND } X = \bar{X}$
 $\overline{X \cdot X}$
 Ex. $X \text{ NOR } X = \bar{X}$
 $\overline{X + X}$
 $\left. \begin{aligned} * \bar{X} &= X \text{ NAND } X \\ &= X \text{ NOR } X \\ &= X \text{ NAND } 1 \\ &= X \text{ NOR } 0 \end{aligned} \right\}$
DeMorgan's Theorem ←
 ① $\overline{A_1 \cdot A_2 \cdot A_3 \cdots A_n} = \bar{A}_1 + \bar{A}_2 + \cdots + \bar{A}_n$
 ② $\overline{A_1 + A_2 + \cdots + A_n} = \bar{A}_1 \cdot \bar{A}_2 \cdot \cdots \cdot \bar{A}_n$

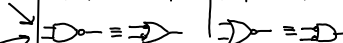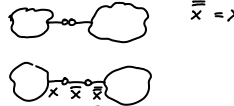Two variables
 $\overline{X \cdot Y} = \bar{X} + \bar{Y}$ $\overline{X + Y} = \bar{X} \cdot \bar{Y}$

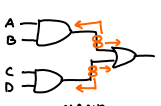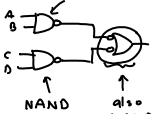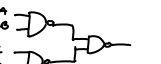 Ex. $\overline{\bar{A}BC} = \bar{\bar{A}} + \bar{B} + \bar{C} = A + \bar{B} + \bar{C}$
 D.T.
 $\overline{\bar{A} + B + C} = \overline{\bar{A}} \cdot \bar{B} \cdot \bar{C} = A \cdot \bar{B} \cdot \bar{C}$
 D.T.
 "play with bubble"

 $\overline{\bar{X}} = X$

Suppose you have

 NAND

 NAND also NAND


Conclusion
 ① You can create a bubble (→) or nothing and
 ② When you pass through an AND gate (AND ↔ OR)
 ③ Sometimes, you have an isolated final design, as "→" "0" is not "→" is .

te a pair of
 →) out of
 move them.

ove a bubble ("0")
 AND gate or
 , the gate changes

u may want to leave
 bubble in your
 answer. Write it
 in stead of "0".

a gate. } No
 a NOT gate. } pun
 intended.

Product term: $A\bar{B}C$,
 is a single
 literal or a
 product of two
 or more literals.

sum term: is a single literal
 or a sum of two
 or more literals.

Ex. $A + \bar{B} + C$
 $A + C$

DeMorgan's
 theorem

Caution
 \overline{ABC} is not a
 product term.

Caution: $\overline{A+B+C}$ is not
 a sum term.

Ex. $A + \overline{A\bar{B}C}$ is not a sum term.
 not literals.

$A + \overline{A\bar{B}C}$ is not a product term.

Q: When does $\overline{A\bar{B}C} = 1$?

$A = 1$
 $\bar{B} = 1$
 $C = 1$

Therefore, $\overline{A\bar{B}C} = 1$ iff $(A, B, C) = (1, 0, 1)$
 if and only if

Q: When does $\overline{A+B+C} = 0$?

$A = 0$
 $\bar{B} = 0$
 $C = 0$ } \Rightarrow iff $(A, B, C) = (0, 1, 0)$

Sum-of-Products (SOP)
 is a sum of product terms.

Ex $A\bar{B} + ABC$,
 $AB + C$,
 $ABC + CDE$

Ex. Develop a truth table for
 $X = A\bar{B} + ABC$

A	B	C	$A\bar{B} + ABC$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

$A\bar{B} = 1?$
 $A = 1$
 $B = 0$

$ABC = 1?$
 $A = 1$
 $B = 1$
 $C = 1$

Remark:

- $A\bar{B}$ corresponds to two "1"s in the truth table.
- ABC corresponds to a unique "1" (or a unique row) in the truth table.

Next time: standard SOP

Free to choose
 the value of "C".

