

# Quiz 3

- Closed book. Closed notes. No calculator.
- Separate into groups of no more than three persons.

Draw the complete state diagrams for linear feedback shift registers (LFSRs) using the following polynomials. Does either LFSR generate an m-sequence?

- $x^4+x^3+x^2+x+1$
- $x^4+x^3+1$


Remark: This was an actual final exam problem @ Cornell

# Quiz 3 Solution

Monday, January 25, 2010  
9:43 PM

①
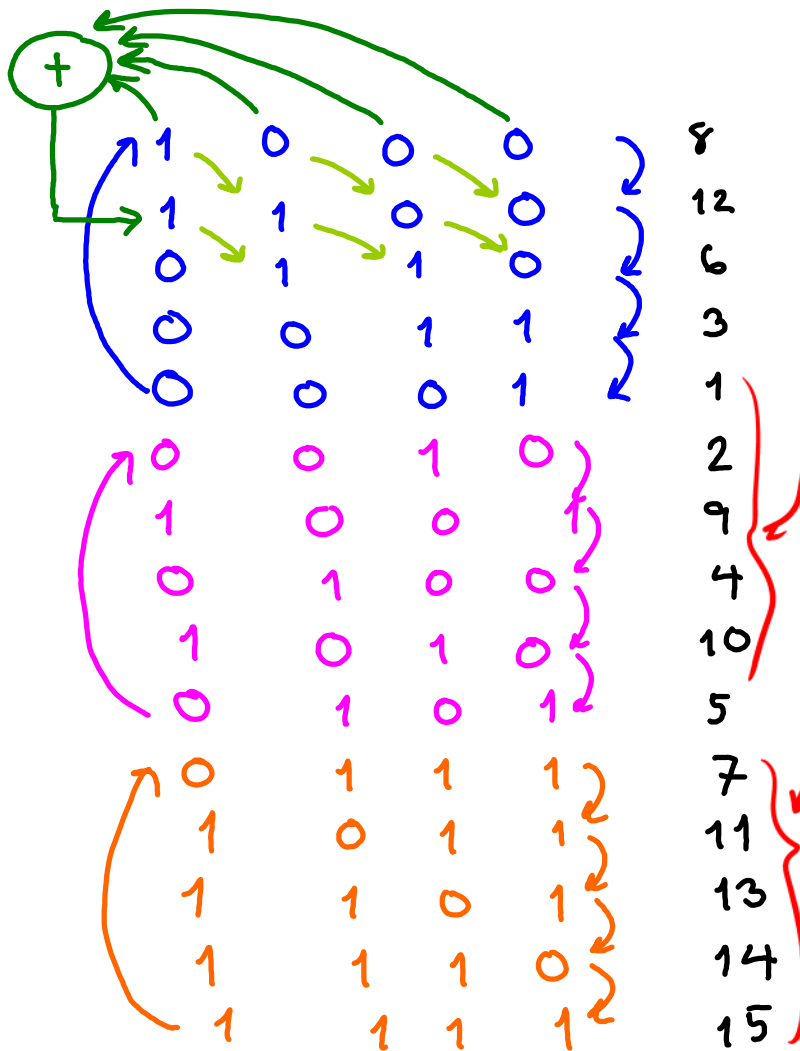
$$1 + \alpha + \alpha^2 + \alpha^3 + \alpha^4$$





Note that because the question says "complete" state diagrams, we need to show these two cycle as well.

It does not generate  $m$ -sequence because no cycle goes through all non-zero states.

②

$$1 + \alpha^3 + \alpha^4$$

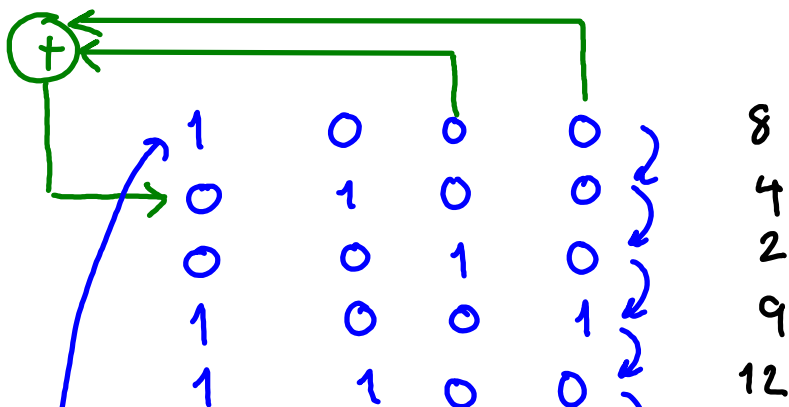

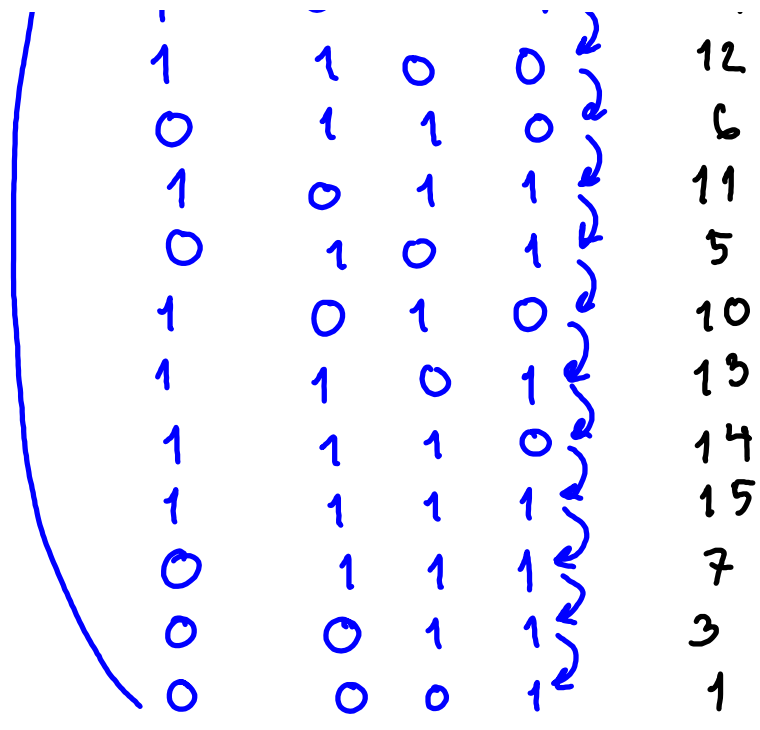

It generates an m-sequence because the cycle covers all non-zero state.