


**School of Information, Computer and Communication Technology**  
**Sirindhorn International Institute of Technology**  
**Thammasat University**

---

**ECS204 Quiz 7 Sample**


---

1.

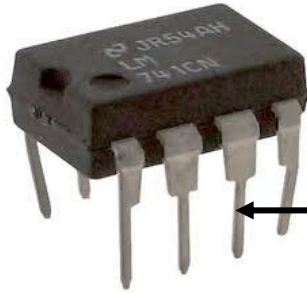

What is the pin number of this leg?

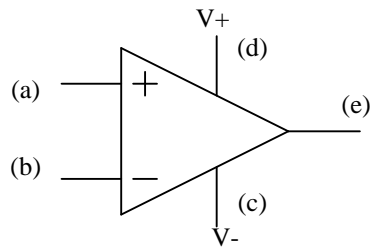2. Find the pin numbers which correspond to the indicated terminals in the figure below.



	(a)	(b)	(c)	(d)	(e)
Corresponding Pin Number				7	